

I. RC Circuit - I think you can do all of these.

The basic starting point is to have a voltage loop such that

$$V_{in} - V_R = V_{out} = V_C$$

and assume V_{out} doesn't draw any current

also $V_C = \frac{Q}{C}$ ← charge on capacitor

and $i_R = \dot{Q}$.

Then solve the resulting first order linear differential equation with an exponential function.

I am sure this will be explained in a circuits text.

(In the "Lab" notice $37\% = \frac{1}{e} = e^{-1}$

and $63\% = 1 - e^{-1}$.)

2. Differentiator - again assume V_{out} draws no current.

$$V_{IN} - V_C = V_{out}$$

but V_{out} is also equal to iR

$$\text{and } V_C = \frac{Q}{C} = \frac{1}{C} \int i dt + k$$

↑
some
integration
constant

$$V_{IN} - \frac{1}{C} \int i dt + k = iR$$

Take the time derivative

$$\frac{dV_{IN}}{dt} - \frac{1}{C} i = R \frac{di}{dt}$$

$$\frac{dV_{IN}}{dt} - \frac{1}{C} \frac{V_{out}}{R} = R \frac{di}{dt}$$

$$V_{out} = RC \left(\frac{dV_{IN}}{dt} - R \frac{di}{dt} \right)$$

$$= RC \left(\frac{dV_{IN}}{dt} - \frac{dV_{out}}{dt} \right)$$

if $\frac{dV_{out}}{dt} \ll \frac{dV_{IN}}{dt}$ then $V_{out} = RC \frac{dV_{IN}}{dt}$

Essentially you are running a high pass filter at low frequency. Not much signal gets through but what does is proportional to the time derivative of V_{IN} .

(3) Integrator (The circuit shown in (1))

$$\underbrace{V_{IN} - iR}_{\substack{\uparrow \\ \text{integrates}}} = V_{OUT} = V_C = \frac{Q}{C}$$

$$\int V_{IN} dt - R \int i dt = \int V_{OUT} dt$$

\uparrow
 $= CV_{OUT}$

$$RC V_{OUT} = \int (V_{IN} - V_{OUT}) dt$$

$$V_{OUT} = \frac{1}{RC} \int (V_{IN} - V_{OUT}) dt$$

$$\approx \frac{1}{RC} \int V_{IN} dt \quad \text{if } V_{OUT} \ll V_{IN}$$

essentially running a low pass filter at high frequency charges (integral of current) are building up on the capacitor to give some V_{OUT} but the capacitor largely "shorts" the circuit at high frequency forcing V_{OUT} small in magnitude

(4) Low-Pass Filter

we will see in class

$$\text{dB} = 20 \log_{10} \frac{V_{\text{out}}}{V_{\text{in}}}$$

(so 3 dB actually tells about power (V^2) amplification or attenuation)

So solve this formula to find $V_{\text{out}}/V_{\text{in}}$ for 3dB (or -3dB)

(because for this passive filter $|V_{\text{out}}| < |V_{\text{in}}|$)
we now have sinusoidal-in and sinusoidal-out so you can use the expressions for complex impedance.

$$V_{\text{out}} = \frac{Z_c}{Z_c + R} V_{\text{in}}$$

$$\text{sub in } Z_c = \frac{1}{j\omega C}$$

and find the magnitude of $\frac{Z_c}{Z_c + R}$ to give

you the correct $|V_{\text{out}}|/|V_{\text{in}}|$ for -3dB

And also find phase. $x + jy = R e^{i\phi}$ $R = \sqrt{x^2 + y^2}$, $\phi = \tan^{-1}(\frac{y}{x})$

The sketch will be Amplitude ($\frac{|V_{\text{out}}|}{|V_{\text{in}}|}$) and ϕ vs f

(5) now have $V_{out} = \frac{R}{R + Z_c} V_{IN}$

(6) V_{AC} is quoted as root mean squared (RMS)

and that is also what a voltmeter on AC measures

(if $V(t) = V_0 \sin \omega t$)

$$\begin{aligned} \text{then } V_{RMS} &= \left(\frac{1}{T} \int_0^T (V_0 \sin \omega t)^2 dt \right)^{1/2} \\ &= \frac{1}{\sqrt{2}} V_0 \end{aligned}$$

The high-pass filter is shown in (5). Low-pass in (4)

(7) Maybe use nodal voltages for this one... (A)