

Physics 323

Experiment # 9 - FET Characteristics and Circuits

Introduction

This is a “quick and dirty” introduction to FET’s through building and examining a ‘pot-pourri’ of circuits. You will use a 2N5485 which is a n-channel JFET (data attached). The connections are




Prelab

- Give the relationship between I_D and V_{GS} for a JFET and sketch the curve.
- Define the mutual transconductance, g_m , and derive a relationship for g_m from (a)
- Sketch the curves for I_D vs. V_{DS} and indicate on them where it would be suitable to operate the FET as (i) a current source (ii) a variable resistor.
- Draw a small signal model for a FET and derive a relationship for the voltage gain of a source follower.

Lab

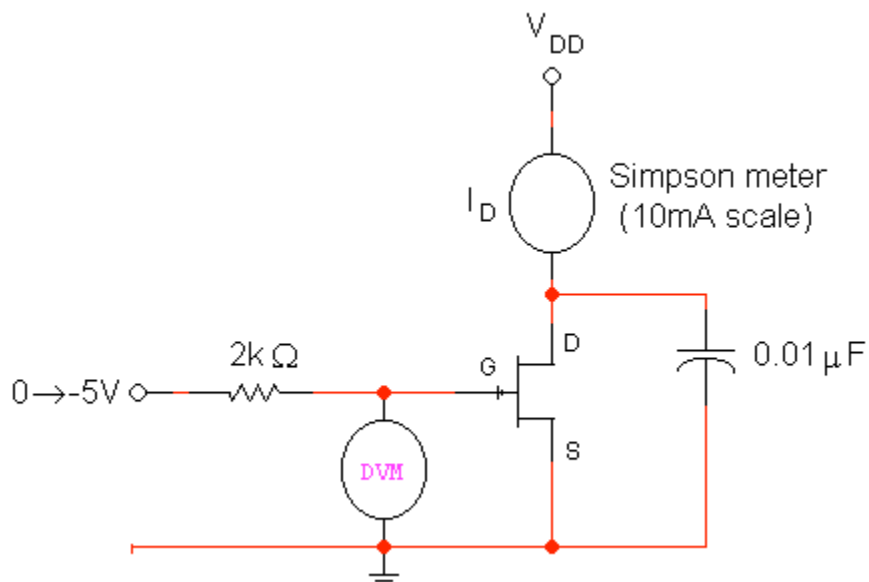
(1) FET Characteristics

Connect up the following circuit and measure I_D and V_{GS} to determine I_{DSS} and $V_P(=V_T)$. Compare with manufacturer’s specifications.



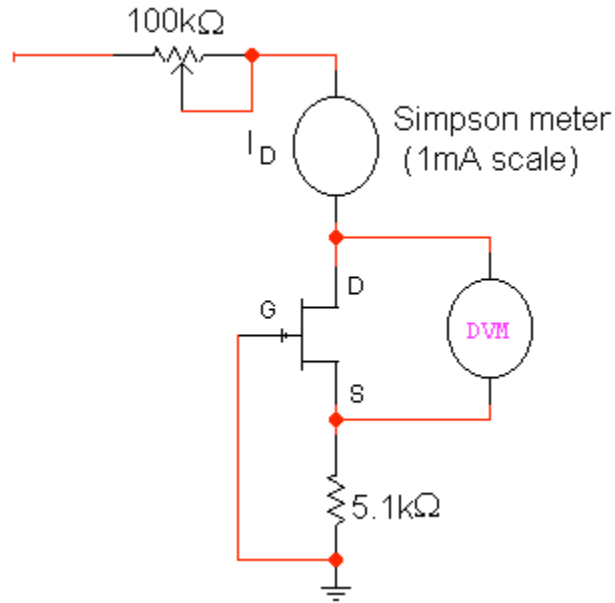(2) FET Current Source


Vary the resistance of the load and measure V_{DS} and I_D . Determine V_{DS} when the constant current behaviour breaks down - is this what you would expect from (1)?



(3) Source Follower

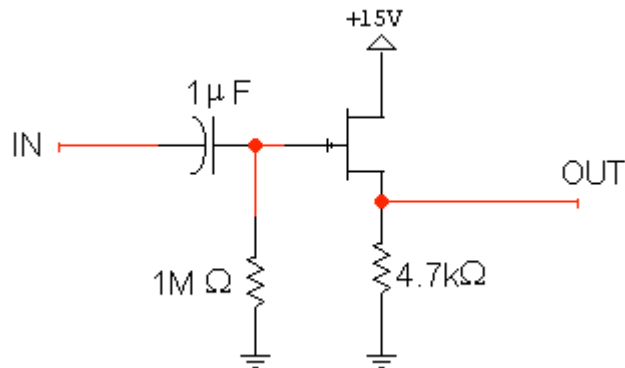
(a) Simple follower

Drive the source follower with a sine wave (~ 1 V p-p at 1 kHz). Measure voltage gain and V_S . Infer g_m (transconductance) at this quiescent I_D . Compare with data sheet g_m (measured at $V_{GS} = 0$ V) and use the data sheet value to predict the g_m under your circuit conditions for comparison with your measured value.



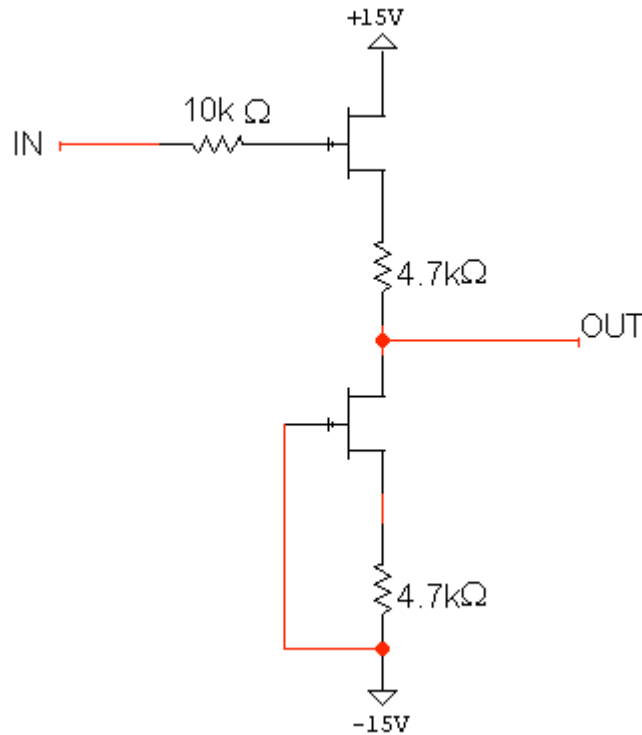(b) Follower with current source load


Measure gain with a 1 V, 1 kHz signal. Measure DC offset of the output. Why should it be zero and why isn't it?




(4) FET as a variable resistor

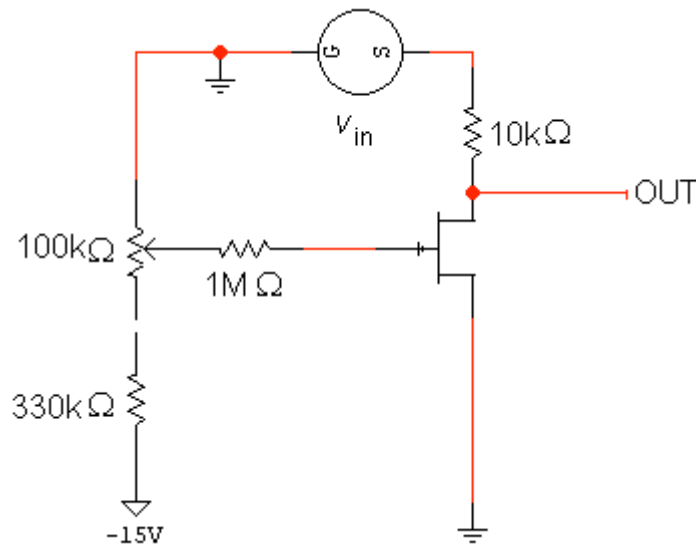(a) Simple attenuator

This circuit operates in the “linear region” i.e. not the “current source region”. Drive the circuit with a small sine wave (~0.2 V at 1 kHz). Adjust the potentiometer and notice results i.e. measure gain and check distortion (more easily seen with triangular wave). Explain any distortion.



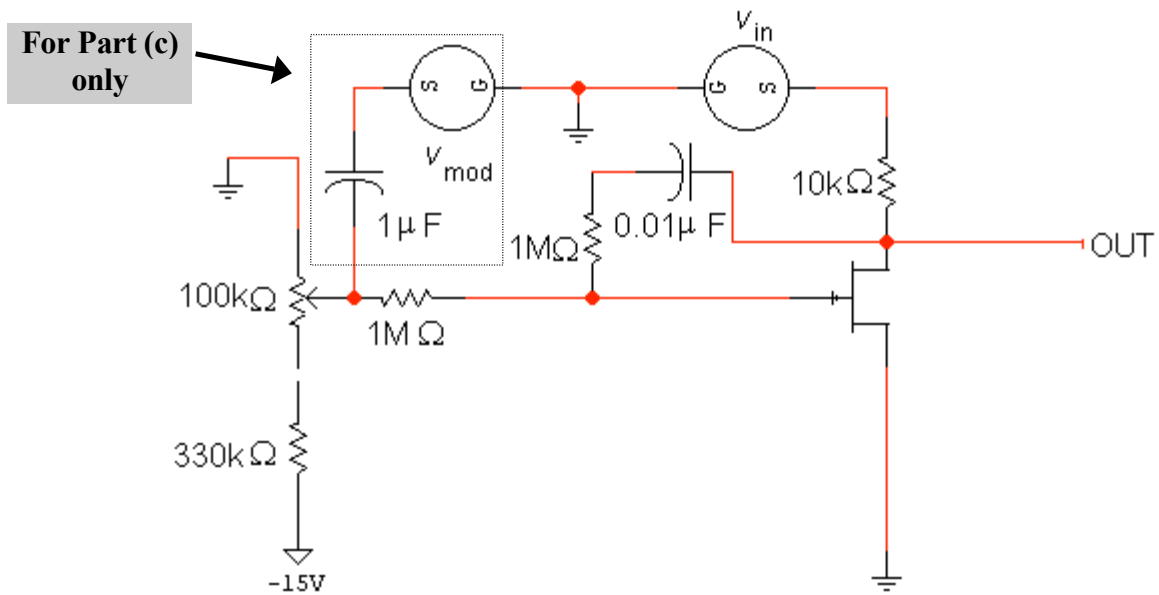- (b) Compensated attenuator
 Compare performance of this circuit with (a).



- (c) Amplitude modulation

(a) and (b) have shown that we can vary attenuation with a potentiometer!! However, the FET is useful since we can vary attenuation with a voltage. To demonstrate this let a second function generator drive the point that you drove with the potentiometer, so that it varies (modulates) the attenuation periodically. Try $f_{mod} \sim 50\text{ Hz}$, and $V_{mod} \sim 0.2\text{ V}$ and watch the output (trigger the scope on the modulation).