

$$V_{\text{amplitude}} = \sqrt{2} V_{RMS} \quad (1)$$

$$A_V = \frac{V_{out}}{V_{in}} \quad (2)$$

$$A_V(\text{ideal}) = \frac{V_{out,OC}}{V_{in}} \quad (3)$$

$$V = IR \quad (4)$$

$$R_{Th} = R_N = \frac{V_{OC}}{I_{SC}} \quad (5)$$

$$\text{Gain (dB)} = 10 \log_{10} \frac{P_2}{P_1} \stackrel{*}{=} 20 \log_{10} \frac{V_2}{V_1} \quad (6)$$

$$Z_R = R \quad (7)$$

$$Z_C = (j\omega C)^{-1} \quad (8)$$

$$Z_L = j\omega L \quad (9)$$

$$\text{if } z = x + jy = re^{j\phi} \text{ then} \quad (10)$$

$$r = \sqrt{x^2 + y^2} \quad \phi = \text{Tan}^{-1} \left( \frac{y}{x} \right) \quad (11)$$

$$x = r \cos \phi \quad y = r \sin \phi \quad (12)$$

$$\text{Gain (closed-loop)} = \frac{A}{1 + AB} \quad (13)$$

$$f_{3dB} = (2\pi RC)^{-1} = (2\pi\tau)^{-1} \quad (14)$$

$$\text{Gain (non-inverting)} = \frac{R_1 + R_2}{R_2}, (R_1 \text{ connected to the output}) \quad (15)$$

$$\text{Gain (inverting)} = -\frac{R_1}{R_2}, (R_1 \text{ connected to the output}) \quad (16)$$

$$V_{out}(t) = -\frac{1}{RC} \int_0^t dt' V_{in}(t') + \text{constant} \quad (17)$$

$$V_{out} = -RC \frac{dV_{in}(t)}{dt} \quad (18)$$

$$V_{out} = -(V_1 + V_2) \frac{R_1}{R_2}, (R_1 \text{ connected to the output}) \quad (19)$$

$$V_{out} = -(V_1 - V_2) \frac{R_1}{R_2}, (R_1 \text{ connected to output and ground}) \quad (20)$$

$$(\text{Gain})(\text{Bandwidth}) \sim (\text{unity gain bandwidth}) \quad (21)$$